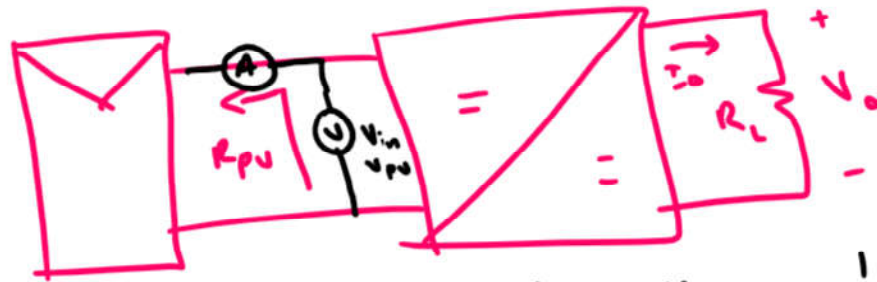


# PV interfacing

Monday, March 15, 2021 9:21 AM

## Boost Converter



$$R_{pv} = \frac{V_{pv}}{I_{pv}}$$



$$\frac{V_o}{V_{in}} = \frac{V_o}{V_{pv}} = \frac{1}{1-D} = \frac{I_{pv}}{I_o}$$

$$R_{pv} = \frac{(1-D) V_o}{\frac{I_o}{(1-D)}} = (1-D)^2 \frac{V_o}{I_o} = (1-D)^2 R_o$$

$$R_{pv} = (1-D)^2 R_o$$

if  $D=0$   
 $D=!$

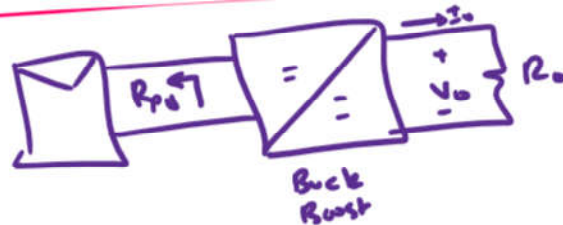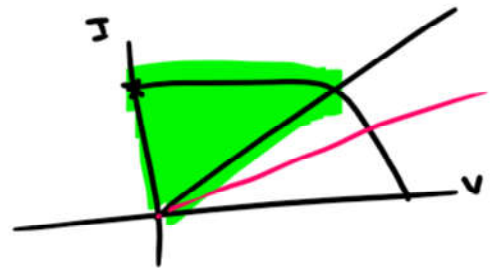if  $R_o < R_{pv}$  then  
boost interface can't track the MPP.





$$\frac{I_{pv}}{I_o} = \frac{V_o}{V_{pv}} = \left( \frac{D}{1-D} \right) \rightarrow R_{pv} = \frac{V_{pv}}{I_{pv}}$$

$$R_{pv} = \frac{\left( \frac{1-D}{D} \right) V_o}{\frac{D}{(1-D)} I_o} = \left( \frac{1-D}{D} \right)^2 R_o$$

if  $D=0$   $R_{pv}=\infty$



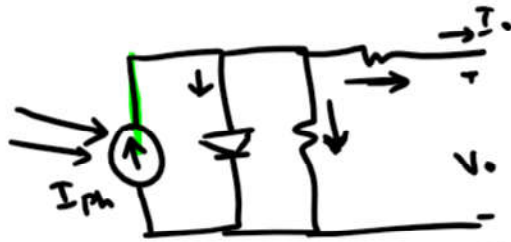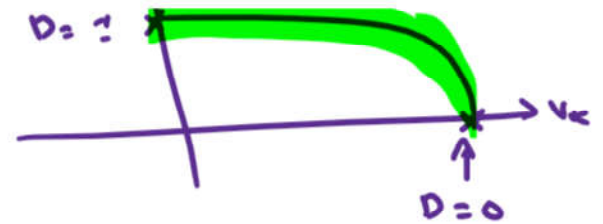$9/ \quad D=0 \quad R_{ps}=\infty$   
 $D=? \quad R_{ps}=0$




Buck  $\rightarrow D = \sqrt{\frac{R_o}{R_{ps}}} = \sqrt{\frac{1}{4.8}}$

$D = 0.45$

Boost  $\rightarrow D = 1 - \sqrt{\frac{R_{ps}}{R_o}}$

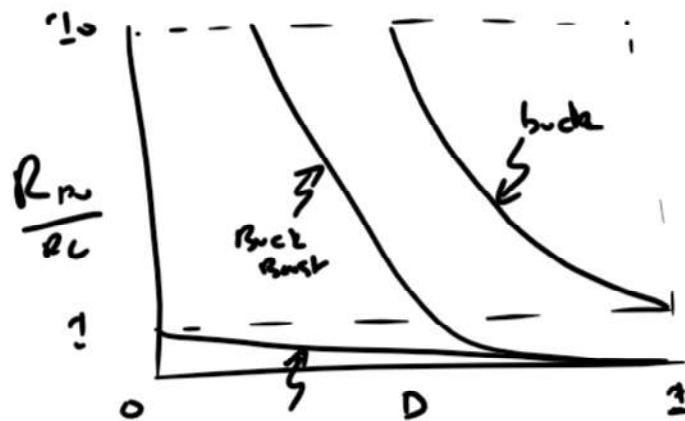Buck-Boost  $\rightarrow D = \frac{1}{1 + \sqrt{\frac{R_{ps}}{R_o}}}$






Buck  $R_{ps} = \frac{R_L}{D^2}$

Boost  $R_{ps} = R_L (1-D)^2$

$\rightarrow$  If we use buck converter for PV, a large o/p Capacitor is required.

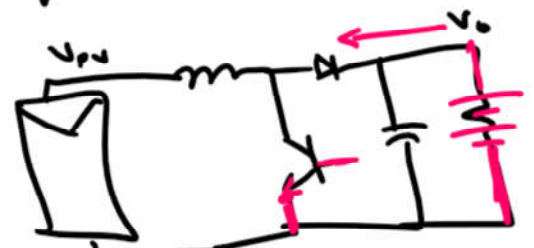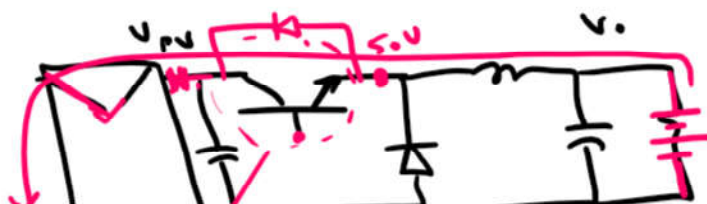$\rightarrow$  Boost converter a large o/p capacitor is required.



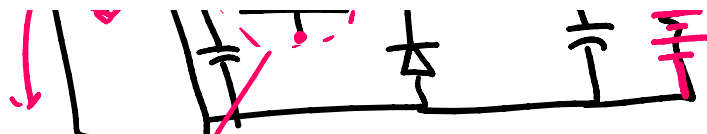

$$V_o < V_{pv}$$

$$I_o > I_{pv}$$

high side driver  
Bootstrap circuitry is required




$$V_o > V_{pv}$$

$$I_o < I_{pv}$$


Low side driver.

## Converter eq. circuits

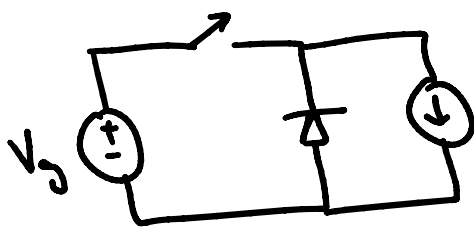


represent continuous conduction of inductor current.

→ Buck

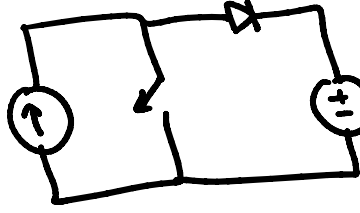


→ Boost

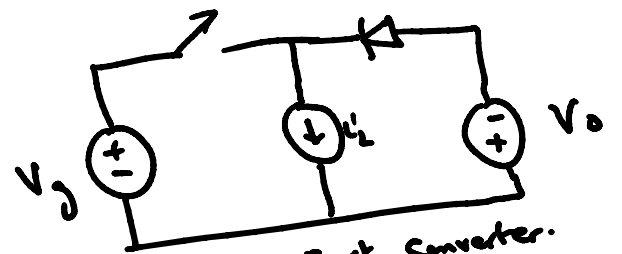CCM of inductor which is placed at the q/p.





Buck-Boost Converter.

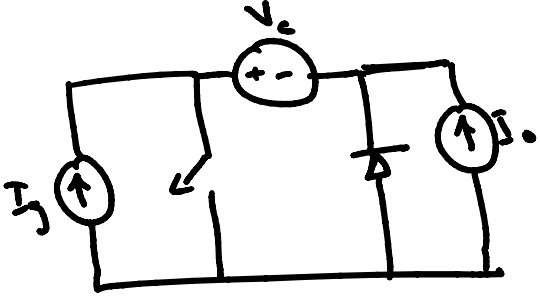


Cuk converter.

## Chapter #3

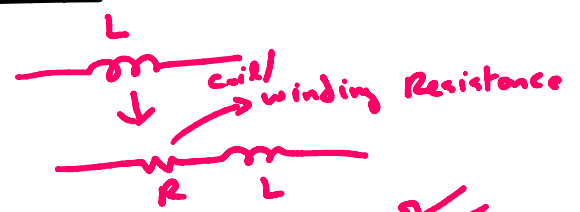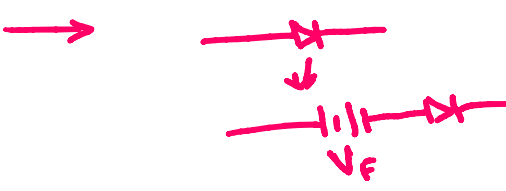


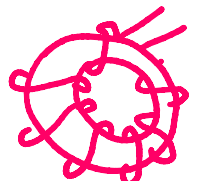
→ include non-idealities of components.  
— / model concept.



- Include non-idealities of components.
- DC Transformer model concept.



## DC Transformer model

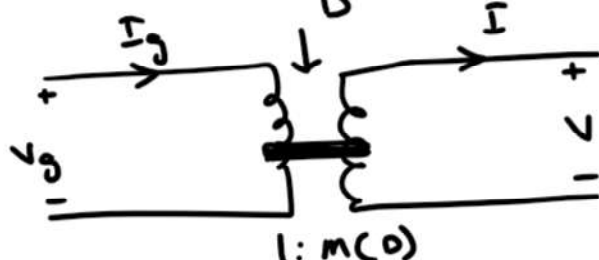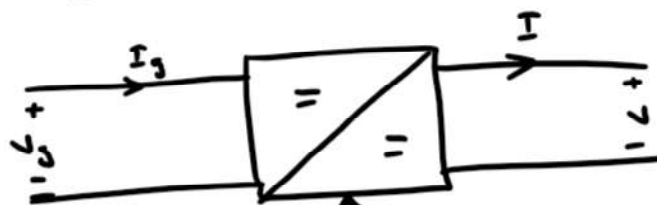


$$P_{in} = P_{out}$$

$$V_g I_g = I V \quad \text{--- (A)}$$

$$V = V_g (m(D)) \quad \text{--- (B)}$$


$$I_g = I (m(D)) \quad \text{--- (C)}$$

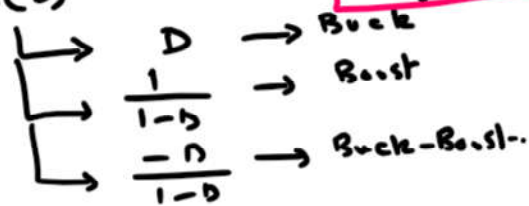

What is  $m(D)$


For  $V_o = V_g$   $\downarrow$

For  $I_g = I_o$   $m(D)$   $\downarrow$

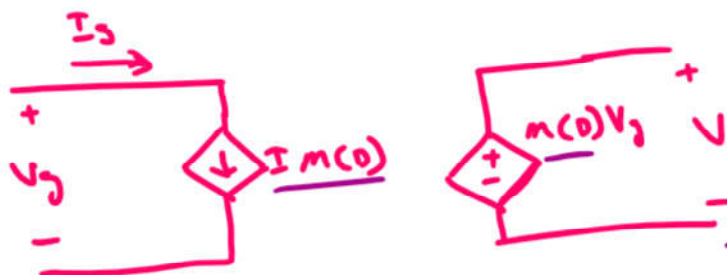

To model a converter like a Tlf with all the

rules.

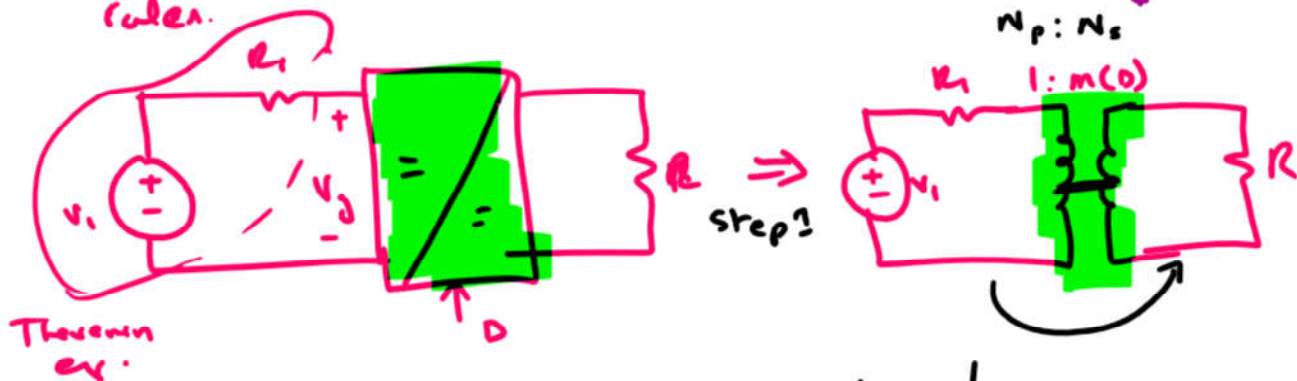

Step 2: Push the g/p to the o/p.  
on sec side  $m(D) V_i$

Step 2 - Pushing it in

$$\begin{array}{lcl} V_1 & \xrightarrow{\text{on sec side}} & m(\omega) V_1 \\ I_1 & \xrightarrow{\text{on sec side}} & \frac{I_1}{m(\omega)} \end{array}$$



$$V_2 = \left( \frac{N_2}{N_1} \right) V_1$$

$$I_2 = \left( \frac{N_1}{N_2} \right) I_1$$

$$R_2 = \frac{V_2}{I_2} = \left( \frac{N_2}{N_1} \right)^2 \frac{V_1}{I_1}$$

$$R_2 = \left( \frac{N_2}{N_1} \right)^2 R_1$$



$$\downarrow (m(\omega))^2 R_1$$



$$V = \frac{m(\omega) V_1 \times R}{R + m^2(\omega) R_1}$$